

Capacitors

Have a go at the following exam questions.

OCR A, G485, Jun 10

- 1 (a) Define *capacitance*.

.....
..... [1]

- (b) Fig. 1.1 shows a circuit consisting of a resistor and a capacitor of capacitance $4.5\ \mu\text{F}$.

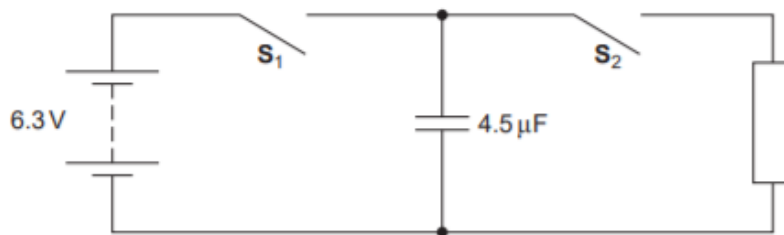


Fig. 1.1

Switch S_1 is closed and switch S_2 is left open. The potential difference across the capacitor is 6.3V.

Calculate

- (i) the charge stored by the capacitor

charge = μC [1]

- (ii) the energy stored by the capacitor.

energy = J [2]

(c) Switch S_1 is opened and switch S_2 is closed.

(i) Describe and explain in terms of the movement of electrons how the potential difference across the capacitor changes.

.....

 [3]

(ii) The energy stored in the capacitor decreases to zero. State where the initial energy stored in the capacitor is dissipated.

.....
 [1]

(d) Fig.1.2 shows the $4.5\mu\text{F}$ capacitor now connected in parallel with a capacitor of capacitance $1.5\mu\text{F}$. Both switches are open and both capacitors are uncharged.

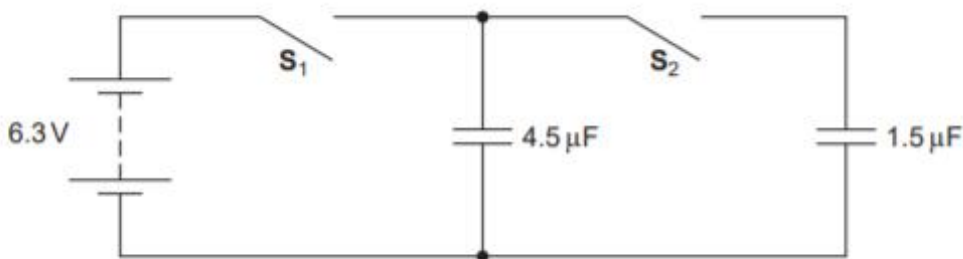


Fig. 1.2

Switch S_1 is closed. The potential difference across the $4.5\mu\text{F}$ capacitor is now 6.3V. Switch S_1 is opened and then switch S_2 is closed.

(i) Calculate the total capacitance of the circuit when S_2 is closed.

capacitance = μF [1]

(ii) Calculate the final potential difference across the capacitors.


potential difference = V [2]

[Total: 11]



A3. (a) Calculate the capacitance of the capacitor shown. [2]

$$C = \frac{\epsilon_0 A}{d}$$

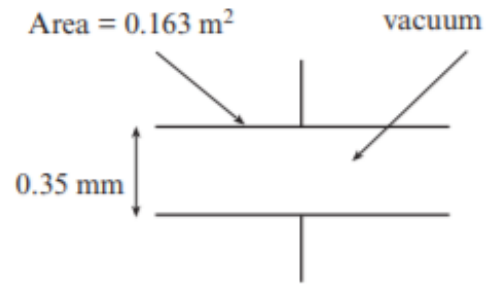

.....

.....

.....

(b) The capacitor is charged so that there is a p.d. of 1.2 kV across the plates. Calculate

(i) the charge stored, [1]

.....

.....

(ii) the energy stored in the capacitor. [1]

.....

.....

(c) The capacitor is discharged through a 670 kΩ resistor. Calculate the time the capacitor takes to lose half its charge. [3]

.....

.....

.....


(d) Explain briefly whether or not the time the capacitor takes to lose half its energy is longer or shorter than your answer to (c). [2]

.....

.....

.....

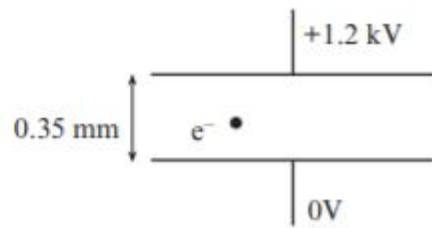- (e) An electron is located between the plates of the charged capacitor. Show that the acceleration experienced by the electron is approximately $6 \times 10^{17} \text{ m s}^{-2}$. [3]



- (f) The electron starts from rest halfway between the plates.

- (i) Use the acceleration ($6 \times 10^{17} \text{ m s}^{-2}$) to calculate the speed of the electron when it strikes the upper plate of the capacitor. [2]

- (ii) Show that the speed of the electron (when it strikes the upper plate of the capacitor) corresponds to a kinetic energy of 0.6 keV and explain briefly another method for obtaining this answer of K.E. = 0.6 keV. [3]

- (iii) Calculate the time the electron takes to travel to the upper plate. [3]

Edexcel IAL, Unit 4, Jun 2011

- 13 A student needs to order a capacitor for a project. He sees this picture on a web site accompanied by this information: capacitance tolerance $\pm 20\%$.



Taking the tolerance into account, calculate

- (a) the maximum charge a capacitor of this type can hold.

(3)

.....

.....

.....

.....

.....

Maximum charge =

- (b) the maximum energy it can store.

(2)

.....

.....

.....

.....

Maximum energy =

(Total for Question 13 = 5 marks)